

MIPS in VHDL

Booker A Robinson

January 2025

Contents


1	Introduction	2
2	Dissecting MIPS	2
2.1	Registers	4
2.2	Control	4
2.2.1	Conditional Branching	4
2.3	Decoding R-type Instructions	4
2.4	Decoding I-type Instructions	5
2.5	Decoding J-type Instructions	5
2.6	Understaning ALU OP	5
2.7	ALU Control	6
3	Designing the CPU	6
3.1	Designing the Instruction Decoder (Controller)	6
3.2	Designing the Instruction Memory	6
3.2.1	Reading Program from a File	6
3.2.2	Multiplexing the Instruction Memory	7
3.3	Designing the ALU	7
3.4	Designing the Registers	8
3.5	Designing the Data Memory	9
3.5.1	Defining the Memory mapped IO	9
3.6	IO	9
3.7	Segment Display Driver	9
3.8	Connecting all the parts	9
4	Programming with Assembly and Machine Code	9
4.1	Examples	9
4.1.1	Fibonacci	9
4.1.2	Interactive program	10
5	TODO	11
6	Conclusions and Future Work	11

1 Introduction

This document will attempt to distill the implementation of a simple Single-Cycle CPU architecture in VHDL. The architecture that we will be implementing is called MIPS.

2 Dissecting MIPS

 
Here we can see a schematic of the MIPS architecture that we will be implementing.



MIPS architecture schematic [4]



Utilization

 

2.1 Registers

Instruction	Index	Binary	Instruction	Index	Binary
\$zero	0	00000	\$s0	16	10000
\$at	1	00001	\$s1	17	10001
\$v0	2	00010	\$s2	18	10010
\$v1	3	00011	\$s3	19	10011
\$a0	4	00100	\$s4	20	10100
\$a1	5	00101	\$s5	21	10101
\$a2	6	00110	\$s6	22	10110
\$a3	7	00111	\$s7	23	10111
\$t0	8	01000	\$t8	24	11000
\$t1	9	01001	\$t9	25	11001
\$t2	10	01010	\$k0	26	11010
\$t3	11	01011	\$k1	27	11011
\$t4	12	01100	\$gp	28	11100
\$t5	13	01101	\$sp	29	11101
\$t6	14	01110	\$fp	30	11110
\$t7	15	01111	\$ra	31	11111

2.2 Control

The controller takes in the op code of an instruction and outputs control flags for each component in the CPU. Our 12 bit control output will be as follows.

reg_dst	jump	link	branch	mem_read	mem_to_reg	alu_op	mem_write	alu_src	reg_write
0	0	0	00	0	0	000	0	0	0

2.2.1 Conditional Branching

branch	Action
0 0	No branch
0 1	Branch if equal <i>Note: The unconditional relative branch is not used</i>
1 0	Branch if not equal
1 1	Uncondition relative branch

2.3 Decoding R-type Instructions

Instruction	op	rs	rt	rd	shamt	funct	Control
sll \$t2, \$t0, 2	000000	00000	01001	01010	00010	000000	1000000 010 001
srl \$t2, \$t0, 2	000000	00000	01001	01010	00010	000010	1000000 010 001
add \$t2, \$t0, \$t1	000000	01000	01001	01010	00000	100000	1000000 010 001
sub \$t2, \$t0, \$t1	000000	01000	01001	01010	00000	100010	1000000 010 001
and \$t2, \$t0, \$t1	000000	01000	01001	01010	00000	100100	1000000 010 001
or \$t2, \$t0, \$t1	000000	01000	01001	01010	00000	100101	1000000 010 001
nor \$t2, \$t0, \$t1	000000	01000	01001	01010	00000	100111	1000000 010 001
slt \$t2, \$t0, \$t1	000000	01000	01001	01010	00000	101010	1000000 010 001
jr \$ra	000000	01101	00000	00000	00000	001000	1000000 010 001

2.4 Decoding I-type Instructions

Instruction	op	rs	rt	constant/address	Control
beq \$t2, \$t0, 2	000100	01000	01010	0000000000000010	0000100 001 000
bne \$t2, \$t0, 2	000101	01000	01010	0000000000000010	0001000 001 000
addi \$t2, \$t0, 2	001000	01000	01010	0000000000000010	0000000 000 011
slti \$t2, \$t0, 2	001010	01000	01010	0000000000000010	0000000 110 000
andi \$t2, \$t0, 2	001100	01000	01010	0000000000000010	0000000 011 000
ori \$t2, \$t0, 2	001101	01000	01010	0000000000000010	0000000 100 000
lw \$t2, 2(\$t0)	100011	01000	01010	0000000000000010	0000011 000 011
sw \$t2, 2(\$t0)	101011	01000	01010	0000000000000010	0000000 000 011

2.5 Decoding J-type Instructions

Instruction	op	constant/address	Control
j label	000010	00000000000000000000000000000000	0100000 000 000
jal label	000011	00000000000000000000000000000000	0110000 000 000

2.6 Understanding ALU OP

Most resources discussing MIPS implement an extremely limited subset of instructions (MIPS-lite)[5]. Namely; add, sub, and, or, slt, lw, sw, beq, j. This subset allows us to in general to use only two bits to encode aluop. The truth table is usually shown as such:

alu_op1	alu_op0	ALU Instruction
0	0	<i>add</i> [<i>lw</i> , <i>sw</i>]
0	1	<i>sub</i> [<i>beq</i>]
1	0	<i>r - type</i>
1	1	<i>n/a</i>

This resolution is not sufficient for us because we want to implement datapaths for I-type instructions other than lw, sw, and beq. To accomplish this we will add an extra bit to extend the supported I-type instructions according to the following table.

alu_op2	alu_op1	alu_op0	ALU Instruction
0	0	0	<i>add</i>
0	0	1	<i>sub</i>
0	1	0	<i>r - type</i>
0	1	1	<i>and</i>
1	0	0	<i>or</i>
1	0	1	<i>nor</i>
1	1	0	<i>slt</i>
1	1	1	<i>n/a</i>

2.7 ALU Control

ALU Control takes as input the ALU OP and the funct. It outputs the control lines directly to the ALU. With our modified ALU Op signals we will design the ALU control as such.

alu_op	funct	ALU Control	ALU Instruction	shift	shift right
000	xxxxxx	0010	<i>add</i>	0	0
001	xxxxxx	0110	<i>sub</i>	0	0
010	000000	0001	<i>sll</i>	1	0
010	000010	0001	<i>srl</i>	1	1
010	100000	0010	<i>add</i>	1	0
010	100010	0110	<i>sub</i>	1	0
010	100100	0000	<i>and</i>	1	0
010	100101	0001	<i>or</i>	1	0
010	100111	1100	<i>nor</i>	1	0
010	101010	0111	<i>slt</i>	1	0
011	xxxxxx	0000	<i>and</i>	0	0
100	xxxxxx	0001	<i>or</i>	0	0
101	xxxxxx	1100	<i>nor</i>	0	0
110	xxxxxx	0111	<i>slt</i>	0	0
111	xxxxxx	-	<i>n/a</i>	0	0

3 Designing the CPU

3.1 Designing the Instruction Decoder (Controller)

3.2 Designing the Instruction Memory

3.2.1 Reading Program from a File

```
impure function init_ram_hex return array_instructions is
    file text_file: text open read_mode is program_file;

    variable text_line: line;
    variable ram_content: array_instructions;
    variable word: std_logic_vector(31 downto 0);
begin
    for i in 0 to 15 loop
        readline(text_file, text_line);
        bread(text_line, word);
        ram_content(i*4) := word(31 downto 24);
        ram_content(i*4+1) := word(23 downto 16);
        ram_content(i*4+2) := word(15 downto 8);
        ram_content(i*4+3) := word(7 downto 0);
    end loop;
    return ram_content;
end function;
```

```
signal instruction_memory: array_instructions := init_ram_hex;
```

3.2.2 Multiplexing the Instruction Memory


```
instruction <=
    instruction_memory(to_integer(instruction_pointer)) &
    instruction_memory(to_integer(instruction_pointer+1)) &
    instruction_memory(to_integer(instruction_pointer+2)) &
    instruction_memory(to_integer(instruction_pointer+3))
    when (instruction_pointer <= instruction_count*4-4) else x"
00000000";
```

3.3 Designing the ALU

Function	ALU control lines
and	0000
or	0001
add	0010
subtract	0110
set on less than	0111
nor	1100


```
zero_result <= nor result;

with alu_op select
    result <=
        std_logic_vector(unsigned(input1) and unsigned(input2))
    when b"0000",
        std_logic_vector(unsigned(input1) or unsigned(input2))
    when b"0001",
        std_logic_vector(signed(input1) + signed(input2)) when
    b"0010",
        std_logic_vector(signed(input1) - signed(input2)) when
    b"0110",
        set_less_than(input1, input2) when b"0111",
        std_logic_vector(unsigned(input1) nor unsigned(input2))
    when b"1100",
        X"0000" when others;
```

 


ALU

3.4 Designing the Registers

 

Registers

3.5 Designing the Data Memory

 

Data Memory

3.5.1 Defining the Memory mapped IO

3.6 IO

3.7 Segment Display Driver

3.8 Connecting all the parts

4 Programming with Assembly and Machine Code

4.1 Examples

4.1.1 Fibonacci

```
reset:
addi $t0, $zero, 1
addi $k0, $zero, 1
loop: add $t1, $k0, $t0
      add $t0, $k0, $zero
      add $k0, $t1, $zero
      addi $t4, $zero, 28657 # largest 16 bit fibonacci number
      beq $k0, $t4, reset
      j loop
```

```
0010000000000100000000000000000001
0010000000001101000000000000000001
00000011010010000100100000100000
00000011010000000100000000100000
00000001001000001101000000100000
00100000000011000110111111110001
```

```
0001000110011010111111111111001
0000100000000000000000000000010
```

4.1.2 Interactive program

```
# Interactive Program.
# IO:
#   First 16 bits of k0 is the 7 segment display.
#   Second 16 bits of k0 is the led array.
#   First 16 bits of k1 is the switches.
#   Bits 16-20 of k1 are the buttons in the following order:
#   C, U, D, L, R

# Functionality.
# Runs a loop selection.

addi $k0, $0, 1 # Set Segment display 1.
loop_selection:
    srl $t0, $k1, 17 # index Up button.
    andi $t0, $t0, 1 # Bitmask button.
    bne $t0, $zero, run_lights # Check button press.
    addi $k0, $0, 2 # Set Segment display 2.
    srl $t0, $k1, 18 # index Down button.
    andi $t0, $t0, 1 # Bitmask button.
    bne $t0, $zero, increment_segment_display # Check button press.
    addi $k0, $0, 3 # Set Segment display 3.
    srl $t0, $k1, 16 # index Center button.
    andi $t0, $t0, 1 # Bitmask button.
    bne $t0, $zero, fibonacci # Check button press.
    addi $k0, $0, 1 # Set Segment display 1.
    j loop_selection

run_lights:
    addi $t0, $0, 16384 # 1000000000000000
    sll $t0, $t0, 1
    addi $t3, $0, 15
    addi $t1, $0, 0
    run_lights_loop:
        sll $k0, $t0, 1 # Light up each led one at a time.
        sll $t0, $t0, 1
        addi $t1, $t1, 1
        bne $t1, $t3, run_lights_loop
    j loop_selection

increment_segment_display:
    addi $t3, $0, 16
    addi $k0, $0, 0
    increment_segment_display_loop:
        addi $k0, $k0, 1 # Increment the segment display 16 times.
```

```

    bne $k0, $t3, increment_segment_display_loop
    j loop_selection

fibonacci:
    reset:
        addi $t0, $zero, 1
        addi $k0, $zero, 1
    loop: add $t1, $k0, $t0
        add $t0, $k0, $zero
        add $k0, $t1, $zero
        addi $t4, $zero, 28657 # largest 16 bit fibonacci number
        beq $k0, $t4, reset
        j loop
    j loop_selection

```

5 TODO

1. Add jump link and jump reg instructions.
 2. Add MMIO
 3. Fix lw and sw in assembler
 4. Add .data file
 5. Mul
 6. Implement convolution
- Future work
1. vector registers / Instructions (ie. SIMD)

6 Conclusions and Future Work

7 References

- [1] <https://edg.uchicago.edu/~tang/VHDLref.pdf>
- [2] https://staff.fysik.su.se/~silver/digsyst/vhdl_ref.pdf
- [3] <https://digilent.com/reference/programmable-logic/basys-3/start>
- [4] Computer Organization and Design, Patterson & Hennessy [5] https://www.cs.umd.edu/~meesh/cmsc311/clin-cmsc311/Lectures/lecture32/single_control.pdf